



CSE 215 Electronic Design Automation

Research Project

Design, Implementation and Test of a Networks-on-Chip (NoC) Router using VHDL

Supervised by:

Dr. Haytham Azmi

Submitted by:

1. Ahmed Adel Mounir Abd El Latif :: 19P9647
2. Mostafa Lotfy Mostafa :: 18P6000
3. Mohamed Sameh Ahmed :: 17p3033
4. Shehab Mohamed Ibrahim :: 18P7213
5. Yusuf Sameh Fawzi :: 18P1399

Table of Contents

Introduction	3
1. Network on a chip (NoC)	3
2. Router	3
Objectives.....	3
Design Flow	3
1. Design.....	3
2. Simulation	4
3. Synthesis	4
4. Implementation	4
5. Device configuration	4
Literature Review	4
References	4
Design Implementation.....	5
Block Diagram:	6
Schedular Design and FSM Implementation.....	13
Test and Simulation Results	15
Timing Report.....	15
Conclusion.....	21
Task Distribution List.....	21
Appendix A	22
Appendix B	39

Introduction

1. Network on a chip (NoC)

A network on a chip (NOC) is the communication system used on a microchip and it is a network-based subsystem. The network on the microchip is router-based network that sends information between two or more SoC modules by packet switching method.

The network on a chip is a very efficient way of communication as it uses the methods and theories of computer network which made a notable improvement for communication on chip over the traditional crossbar and bus communication architectures. The improvement in the power efficiency and scalability of systems on chip that the NoCs made compared to the many other designs of communication subsystems made the NoC used widely such as in the computer's GPUs that is commonly used in video gaming and computer graphics and accelerating artificial intelligence.

2. Router

The router is the virtual or physical device that forwards information between computer networks in the form of data packets.

A router is connected to two or more lines of data from different internet protocol networks. The network address information in the packet header is read by the router and then the router uses the information in the routing policy to direct the packet to its next destination.

There are five types of routers:

1. Wired router
2. Edge router
3. Core router
4. Virtual router
5. Wireless router

Objectives

The aim of the project is to design, implementation and test a simple router using VHDL.

The project main objective is to design a synthesizable VHDL code for the router and its test bench using the design methodologies studied in EDA course this year.

Design Flow

1. Design

The first step in the design process is to design the code in a machine-readable format, and to do so we will be going to use a CAD (computer aided design) tool, using the model sim free student version offered by mentor graphics.

Model sim is a CAD tool that supports many design entry methods such as schematic capture component netlist, HDL entry (VHDL, Verilog). In this project all the designs are written using VHDL language.

2. Simulation

Once we are done with the design, the next step is to simulate this design to make sure that the design meets all the requirements specified for this project.

3. Synthesis

In this step, our CAD tool will translate the VHDL design we wrote and deduce standard building blocks (such as: adders, latches, registers, ex.) to implement the design. Any delicate change in the VHDL description may result in the inferences in different hardware which may cause different system performance.

4. Implementation

For implementation we will use another CAD tool called Xilinx which will take the design through three processes which are

- **Translate:** process which will convert the netlist generated from the previous process (synthesis step) into a form specific to the target device.
- **Map:** translates the standard building blocks into the specific resources available in the target hardware.
- **Place and Route:** this process complete the map process by placing the specific resources allocated and interconnecting them as the design

5. Device configuration

After verifying the design, then come to the last step where a binary hardware configuration file (bitstream) is generated, then this file will be downloaded on a FPGA.

Literature Review

We are in a global of a totally fast paced changing technology, a big zone of gadgets is included into just one chip. With this being made these devices that is integrated in a chip need to communicate between each other so they can send information and data that are essential for a proper working chip. Back in days the conventional communication used was the bus and the crossbar communication methods which was very slow and was not efficient enough in its power consumption which caused a lot of limitations to our designs. Then the NoC (network on chip) technology was introduced for communication between the different modules integrated on the chip, this new way of communication brought a notable improvement over the old traditional ways of communications. NoC improves system-on-chip scalability and power efficiency of complex SoCs compared to other communication subsystem design, NoC also guarantees flexibility, balance and a better bandwidth. This study targets on diverse implementations of NoC and distinctive approaches of enduring faults of communication among the number of the nodes and henceforth growing the velocity of processing and keep throughput.

By checking the previous research we note that the often primary blocks of the router are similar to the proposed module withinside the file of which it consists of specifically 3 parts (Registers and demultiplexers, First In First Out Registers, and Schedulers)

References

1. Neelakrishnan S. Design and implementation of NoC routers and their application to Prdt-based NoC's.
2. Lotlikar S. Design, implementation and evaluation of a configurable NoC for AcENoCS FPGA accelerated emulation platform. [College Station, Tex.]: [Texas A & M University]; 2011.


Design Implementation


There are 9 modules of NoC router used in this project each of unique functionality and a defined purpose such as:

- 8 bit register
- 8 bit demultiplexer
- Block Ram
- Gray to Binary Converter
- FIFO Controller
- FIFO
- Round Robin scheduler
- Router


Module	Function
M_ROU_01: 8-bit Register	Store packet once arrived and propagates it
M_ROU_02: 4-1 8-bit DeMux	Switch fabric to provide connectivity between inputs and outputs
M_ROU_03: Block Ram	Save data; it contains an array to store data and controlled by the clock
M_ROU_04: Gray Counter	Counts in gray
M_ROU_05: Gray to Binary Converter	Convert gray code to Binary
M_ROU_06: FIFO controller	Validate read or write and check memory availability, read packet header and configure the switch fabric, synchronize router internal modules, control data flow inside the router, apply round robin scheduler
M_ROU_07: FIFO	Work in First in First out sequence, it contains the controller and the memory
M_ROU_08: Round Robin Scheduler	Set data in an organized queue, data passes only at clock cycle
M_ROU_09: Router	route the input data to the correct output port according to the address it gets

Block Diagram:

 


 


gray_to_binary_convertor:1

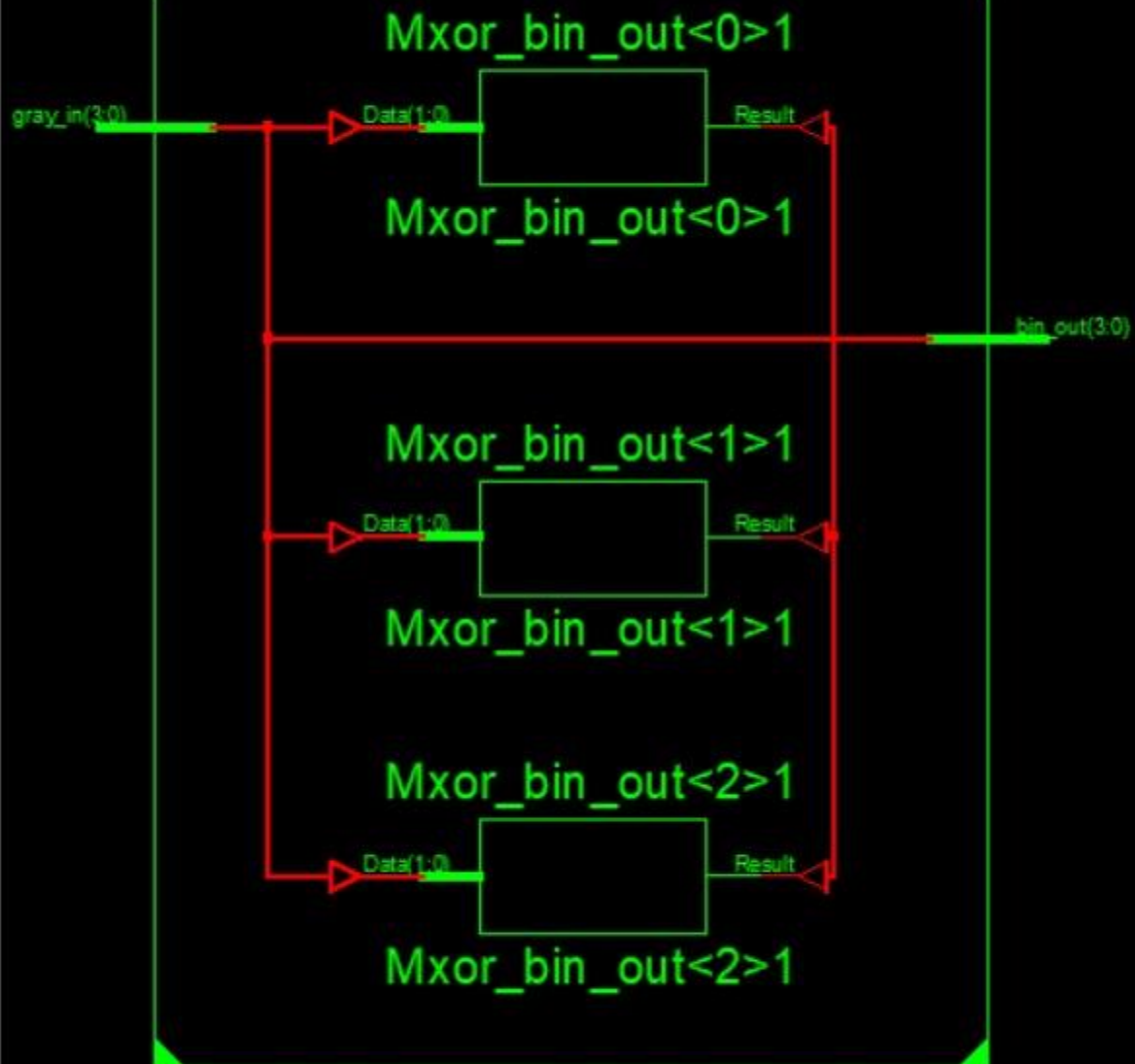


gray_to_binary_convertor

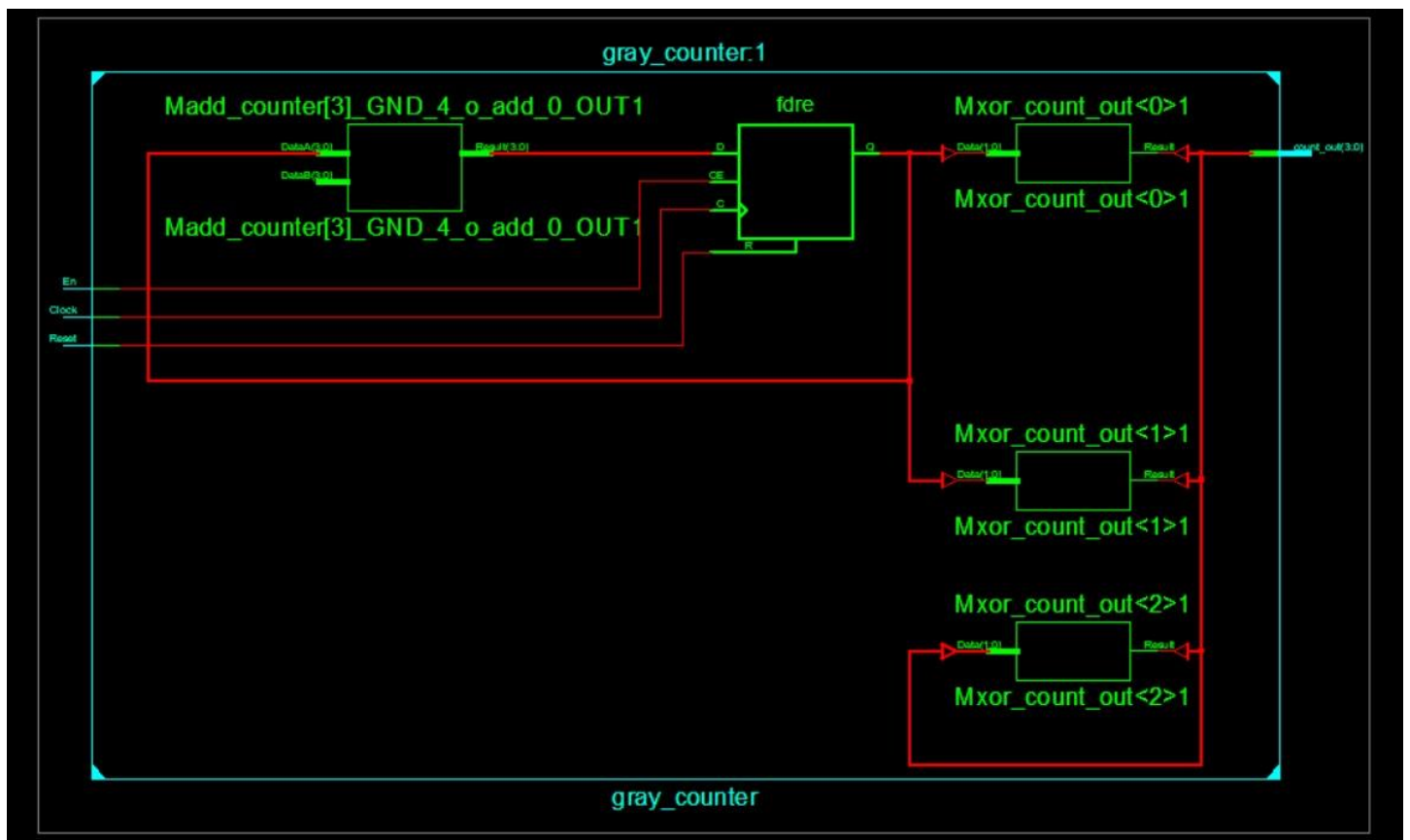

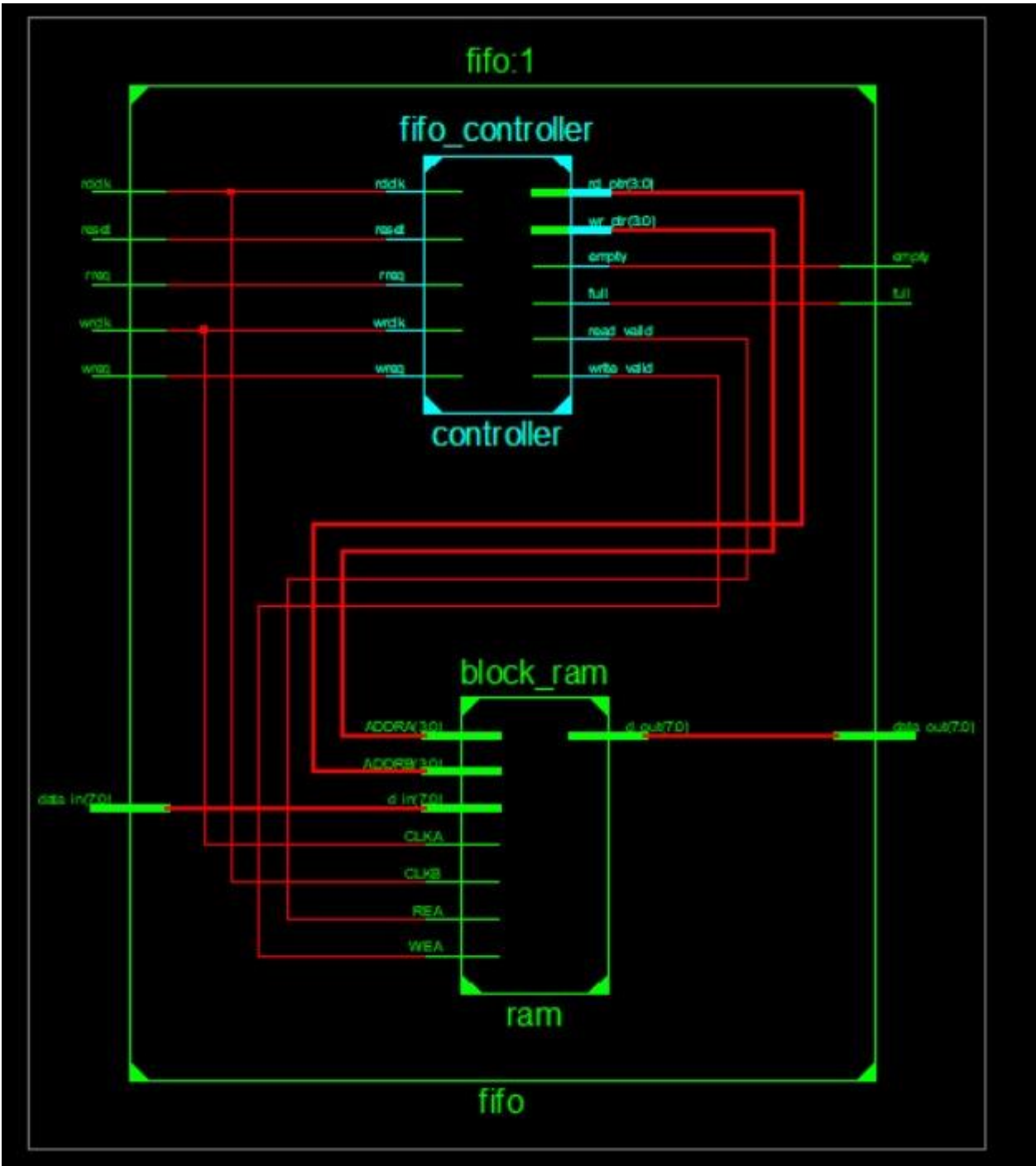

Scheduler Design and FSM Implementation

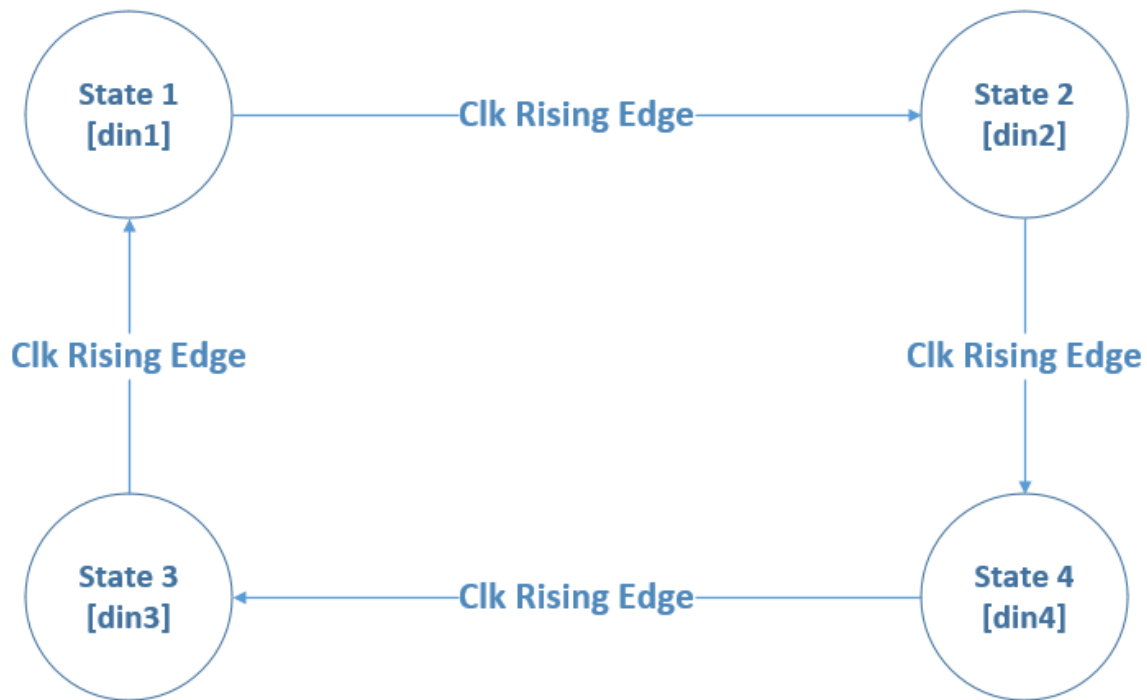

We implemented the FSM of the Round Robin scheduler using the Moore (state-based) coding technique, it consists of 2 processes.

The first process is for updating the current state with each clock cycle.

The second process is for updating the next state and the output based on the current state.

Since the output in the code depends only on the current state, this is a Moore FSM.

Moore (state-based) FSM	Mealy (transition-based) FSM
The output only depends on the current state.	The output depends on the current state in addition to the input.

	1 process	2 processes	3 processes
Mealy	Consists of only 1 process that is sensitive to: <ul style="list-style-type: none">• Clock• Reset• Current state• Input	Consists of 2 processes, the first process is sensitive to: <ul style="list-style-type: none">• Clock• Reset	Consists of 3 processes, the first process is sensitive to: <ul style="list-style-type: none">• Clock• Reset

		<p>The second process is sensitive to:</p> <ul style="list-style-type: none"> • Current state • Input 	<p>The second process is sensitive to:</p> <ul style="list-style-type: none"> • Current state • Input <p>The third process is sensitive to:</p> <ul style="list-style-type: none"> • Current state • Input
Moore	<p>Consists of only 1 process that is sensitive to:</p> <ul style="list-style-type: none"> • Clock • Reset • Current state 	<p>Consists of 2 processes, the first process is sensitive to:</p> <ul style="list-style-type: none"> • Clock • Reset <p>The second process is sensitive to:</p> <ul style="list-style-type: none"> • Current state • Input 	<p>Consists of 3 processes, the first process is sensitive to:</p> <ul style="list-style-type: none"> • Clock • Reset <p>The second process is sensitive to:</p> <ul style="list-style-type: none"> • Current state • Input <p>The third process is sensitive to:</p> <ul style="list-style-type: none"> • Current state

Test and Simulation Results

Tested Feature	Inputs					Expected Output			
	datai1	datai2	datai3	datai4	wr1,wr2, wr3,wr4	datao1	datao2	datao3	datao4
Routing form input port to correct output port	110010 00	100100 01	010101 10	100010 11	1	110010 00	100100 01	010101 10	100010 11
	110110 11	100100 00	011101 01	100011 10	1	100100 00	011101 01	100011 10	110110 11
	110110 10	101100 11	111101 00	000010 01	1	111101 00	000010 01	110110 10	101100 11
	110011 01	110010 10	010101 11	101111 00	1	101111 00	110011 01	110010 10	010101 11

Timing Report

NOTE: THESE TIMING NUMBERS ARE ONLY A SYNTHESIS ESTIMATE.

FOR ACCURATE TIMING INFORMATION PLEASE REFER TO THE TRACE REPORT
GENERATED AFTER PLACE-and-ROUTE.

Clock Information:

-----+-----+-----+		
Clock Signal	Clock buffer(FF name)	Load
-----+-----+-----+		
rdclk	BUFGP	242
wrclk	BUFGP	160
-----+-----+-----+		

Asynchronous Control Signals Information:

No asynchronous control signals found in this design

Timing Summary:

Speed Grade: -3

Minimum period: 2.533ns (Maximum Frequency: 394.726MHz)

Minimum input arrival time before clock: 1.256ns

Maximum output required time after clock: 1.538ns

Maximum combinational path delay: No path found

Timing Details:

All values displayed in nanoseconds (ns)

=====

Timing constraint: Default period analysis for Clock 'rdclk'

Clock period: 2.533ns (frequency: 394.726MHz)

Total number of paths / destination ports: 1011 / 434

Delay: 1.267ns (Levels of Logic = 2)

Source: g2[0].g3[0].queue/controller/gray_read_counter/counter_2 (FF)

Destination: g2[0].g3[0].queue/controller/temp_full (LATCH)

Source Clock: rdclk rising

Destination Clock: rdclk falling

Data Path: g2[0].g3[0].queue/controller/gray_read_counter/counter_2 to g2[0].g3[0].queue/controller/temp_full

	Gate	Net
--	------	-----

Cell:in->out	fanout	Delay	Delay	Logical Name (Net Name)
--------------	--------	-------	-------	-------------------------

FDRE:C->Q	9	0.361	0.416	g2[0].g3[0].queue/controller/gray_read_counter/counter_2 (g2[0].g3[0].queue/controller/gray_read_counter/counter_2)
-----------	---	-------	-------	--

LUT5:I3->O	1	0.097	0.295	g2[0].g3[0].queue/controller/Mmux_b_write_counter[3]_GND_11_o_MUX_17_o1_SW1 (N64)
------------	---	-------	-------	---

LUT6:I5->O	1	0.097	0.000	g2[0].g3[0].queue/controller/Mmux_b_write_counter[3]_GND_11_o_MUX_17_o1 (g2[0].g3[0].queue/controller/b_write_counter[3]_GND_11_o_MUX_17_o)
------------	---	-------	-------	--

LD:D	-0.028			g2[0].g3[0].queue/controller/temp_full
------	--------	--	--	--

Total 1.267ns (0.555ns logic, 0.712ns route)

(43.8% logic, 56.2% route)

Timing constraint: Default period analysis for Clock 'wrclk'

Clock period: 2.375ns (frequency: 421.124MHz)

Total number of paths / destination ports: 816 / 496

Delay: 1.187ns (Levels of Logic = 0)

Source: g2[0].g3[0].queue/controller/write_signal (LATCH)

Destination: g2[0].g3[0].queue/ram/Mram_word1 (RAM)

Source Clock: wrclk falling

Destination Clock: wrclk rising

Data Path: g2[0].g3[0].queue/controller/write_signal to g2[0].g3[0].queue/ram/Mram_word1

Gate Net

Cell:in->out fanout Delay Delay Logical Name (Net Name)

LD:G->Q 7 0.472 0.307 g2[0].g3[0].queue/controller/write_signal
(g2[0].g3[0].queue/controller/write_signal)

RAM32M:WE 0.408 g2[0].g3[0].queue/ram/Mram_word1

Total 1.187ns (0.880ns logic, 0.307ns route)

(74.1% logic, 25.9% route)

Timing constraint: Default OFFSET IN BEFORE for Clock 'wrclk'

Total number of paths / destination ports: 288 / 288

Offset: 1.256ns (Levels of Logic = 2)

Source: wr1 (PAD)

Destination: g2[0].g3[0].queue/ram/Mram_word1 (RAM)

Destination Clock: wrclk rising

Data Path: wr1 to g2[0].g3[0].queue/ram/Mram_word1

	Gate	Net			
Cell:in->out	fanout	Delay	Delay	Logical Name (Net Name)	

IBUF:I->O	39	0.001	0.619	wr1_IBUF (wr1_IBUF)	
LUT4:I1->O	1	0.097	0.279	g1[0].demux_i/Mmux_d_out451 (demux_out<0><3><4>)	
RAM32M:DIC0		0.260		g2[0].g3[3].queue/ram/Mram_word1	

Total		1.256ns (0.358ns logic, 0.898ns route)			
		(28.5% logic, 71.5% route)			

=====
Timing constraint: Default OFFSET IN BEFORE for Clock 'rdclk'

Total number of paths / destination ports: 96 / 96

Offset: 0.923ns (Levels of Logic = 2)
Source: rst (PAD)
Destination: g2[0].g3[0].queue/controller/temp_empty (LATCH)
Destination Clock: rdclk falling

Data Path: rst to g2[0].g3[0].queue/controller/temp_empty

	Gate	Net			
Cell:in->out	fanout	Delay	Delay	Logical Name (Net Name)	

IBUF:I->O	192	0.001	0.825	rst_IBUF (rst_IBUF)	
LUT6:I0->O	1	0.097	0.000	g2[0].g3[0].queue/controller/Mmux_b_read_counter[3]_PWR_11_o_MUX_18_o1 (g2[0].g3[0].queue/controller/b_read_counter[3]_PWR_11_o_MUX_18_o)	
LD:D	-0.028	g2[0].g3[0].queue/controller/temp_empty			

Total	0.923ns (0.098ns logic, 0.825ns route)				
	(10.6% logic, 89.4% route)				

=====

Timing constraint: Default OFFSET OUT AFTER for Clock 'rdclk'

Total number of paths / destination ports: 192 / 32

Offset: 1.538ns (Levels of Logic = 2)
Source: g1[3].scheduler/current_state_FSM_FFd2 (FF)
Destination: datao1<7> (PAD)
Source Clock: rdclk rising

Data Path: g1[3].scheduler/current_state_FSM_FFd2 to datao1<7>

	Gate	Net			
Cell:in->out	fanout	Delay	Delay	Logical Name (Net Name)	

FD:C->Q	34	0.361	0.800	g1[3].scheduler/current_state_FSM_FFd2 (g1[3].scheduler/current_state_FSM_FFd2)	
LUT6:I0->O	1	0.097	0.279	g1[0].scheduler/Mmux_dout11 (datao1_0_OBUF)	
OBUF:I->O		0.000		datao1_0_OBUF (datao1<0>)	

Total	1.538ns (0.458ns logic, 1.080ns route) (29.8% logic, 70.2% route)				

=====

Cross Clock Domains Report:

Clock to Setup on destination clock rdclk

-----+-----+-----+-----+				
Src:Rise Src:Fall Src:Rise Src:Fall				
Source Clock	Dest:Rise Dest:Rise Dest:Fall Dest:Fall			
-----+-----+-----+-----+				

rdclk		1.273		0.897		1.267			
wrclk		1.656				1.818			

-----+-----+-----+-----+-----+

Clock to Setup on destination clock wrclk

-----+-----+-----+-----+-----+

		Src:Rise		Src:Fall		Src:Rise		Src:Fall	
--	--	----------	--	----------	--	----------	--	----------	--

Source Clock |Dest:Rise|Dest:Rise|Dest:Fall|Dest:Fall|

-----+-----+-----+-----+-----+

rdclk		0.706				1.125			
wrclk		1.660		1.187		0.944			

-----+-----+-----+-----+-----+

=====

Total REAL time to Xst completion: 11.00 secs

Total CPU time to Xst completion: 10.66 secs

-->

Total memory usage is 4617572 kilobytes

Number of errors : 0 (0 filtered)

Number of warnings : 4 (0 filtered)

Number of infos : 35 (0 filtered)

Conclusion

NoC router (network on chip router) is used for communication and networking between two or more computer networks and data is sent using the packet switching method. The NoC is very fast for communicating two or more different networks together at a very high speed and very low power consumption compared to other communication designs. We used two CAD tools for all the process done in this project (Model sim, Xilinx).

There were a lot of challenges in the implementation process as there were so many components depending on each other and the connection between them was not that easy as well, but we managed our way through to figure it out.

There were 9 modules in our design each single module of them has its own function. Demux was responsible for the data selection that for implemented using switch cases, Registers was implemented using the if conditions and it was responsible for data transferring, Block Ram in our router was the memory element, FIFO was responsible for mapping the controller with the Block Ram for controlling the flow, Gray to Binary converter was responsible for converting gray to binary code using Xor gates. Finally, our router was implemented by directly mapping all the used modules together.

Task Distribution List

The project workload is distributed equally among all the team members

Appendix A

Module No. M-ROU-01

```
library ieee;
```

```
use ieee.std_logic_1164.ALL;
```

```
use ieee.numeric_std.ALL;
```

```
ENTITY reg IS
```

```
port(Data_in : IN std_logic_vector (7 downto 0);
```

```
Clock : IN std_logic;
```

```
Data_out : OUT std_logic_vector (7 downto 0);
```

```
Clock_En : IN std_logic;
```

```
Reset : IN std_logic);
```

```
end;
```

```
ARCHITECTURE behave OF reg IS
```

```
BEGIN
```

```
process(Clock,Clock_En,Reset) IS
```

```
BEGIN
```

```
    IF Clock'event and Clock = '1' then
```

```
        IF Reset = '1' THEN
```

```
            Data_Out <= (others =>'0') ;
```

```
        ELSIF Clock_En = '1' THEN
```

```
            Data_out <= Data_in;
```

```
        END IF;
```

```
    END IF;
```

```
END PROCESS;
```

```
END;
```

Module No. M-ROU-02

```
library ieee;
```

```
use ieee.std_logic_1164.ALL;
```

```
use ieee.numeric_std.ALL;
```

```
ENTITY demux IS
```

```
PORT (Sel: IN std_logic_vector (1 downto 0);
```

```
En : IN std_logic;
```

```
d_in : IN std_logic_vector ( 7 downto 0);
```

```
d_out1,d_out2,d_out3,d_out4 : OUT std_logic_vector (7 downto 0));
```

```
END;
```

```
ARCHITECTURE behave OF demux IS
```

```
BEGIN
```

```
PROCESS (Sel,En, d_in) IS
```

```
BEGIN
```

```
    IF EN = '1' THEN
```

```
        case (sel) is
```

```
            when "00" => d_out1 <= d_in; d_out2 <= (others => '0');d_out3 <= (others => '0');d_out4 <= (others => '0');
```

```
            when "01" => d_out2 <= d_in; d_out1 <= (others => '0');d_out3 <= (others => '0');d_out4 <= (others => '0');
```

```
            when "10" => d_out3 <= d_in; d_out2 <= (others => '0');d_out1 <= (others => '0');d_out4 <= (others => '0');
```

```
            when "11" => d_out4 <= d_in; d_out2 <= (others => '0');d_out3 <= (others => '0');d_out1 <= (others => '0');
```

```
            when others => d_out1 <= (others => '0'); d_out2 <= (others => '0');d_out3 <= (others => '0');d_out4 <= (others => '0');
```

```
        end case;
```

```
    Else
```

```
        d_out1 <= (others => '0');d_out2 <= (others => '0');d_out3 <= (others => '0');d_out4 <= (others => '0');
```

```
    END IF;
```

END PROCESS;

END;

Module No. M-ROU-03

library ieee;

use ieee.std_logic_1164.ALL;

use ieee.std_logic_unsigned.ALL;

library ieee;

use ieee.std_logic_1164.ALL;

use ieee.STD_LOGIC_unsigned.all;

ENTITY block_ram IS

PORT(d_in : IN std_logic_vector (7 downto 0);

ADDRA,ADDRB :IN std_logic_vector (3 downto 0);

WEA,REA,CLKA,CLKB :IN std_logic;

d_out : OUT std_logic_vector (7 downto 0));

END ENTITY block_ram;

ARCHITECTURE behave OF block_ram IS

TYPE wrm IS ARRAY (0 to 31) OF std_logic_vector (7 downto 0);

SIGNAL word : wrm;

BEGIN

wm : PROCESS (WEA,ADDRA,CLKA,d_in) IS

BEGIN

IF CLKA'event and CLKA = '1' AND WEA = '1' THEN

word(conv_integer(ADDRA)) <= d_in;

END IF;

END PROCESS wm;

rm : PROCESS (REA,ADDRB,CLKB,d_in) IS

BEGIN

IF CLKB'event and CLKB = '1' Then


```

    IF REA = '1' THEN

        d_out <= word(conv_integer(ADDRB));

    end if;

end if;

END PROCESS rm;

END;

```

Module No. M-ROU-04

```

library ieee;

use ieee.std_logic_1164.all;

use ieee.numeric_std.all;

entity gray_counter is

    port

    (

        Clock, Reset, En: in std_logic;

        count_out: out std_logic_vector(3 downto 0)

    );

end entity gray_counter;

```

```

architecture behav of gray_counter is

    signal counter: unsigned (3 downto 0);

begin

    clock_tick: process(Reset, clock, En) is

        begin

            if Clock'event and Clock = '1' then

                if Reset = '1' then

                    counter <= "0000";

                elsif En = '1' then

                    counter <= counter + 1;

                end if;

            end if;

        end if;

    end process clock_tick;

end architecture behav;

```

```

        end process clock_tick;

        count_out(3) <= counter(3);

        count_out(2) <= counter (2) xor counter(3);

        count_out(1) <= counter (1) xor counter(2);

        count_out(0) <= counter (0) xor counter(1);

end architecture;

```

Module No. M-ROU-05

```

library IEEE;

use IEEE.STD_LOGIC_1164.ALL;


entity gray_to_binary_convertor is
Port ( gray_in : in STD_LOGIC_VECTOR (3 downto 0);
      bin_out : out STD_LOGIC_VECTOR (3 downto 0)
      );
end gray_to_binary_convertor;

```

```

architecture behav of gray_to_binary_convertor is
begin
    p1:process (gray_in) is
    begin
        bin_out(3)<= gray_in(3);

        bin_out(2)<= gray_in(3) xor gray_in(2);

        bin_out(1)<= gray_in(3) xor gray_in(2) xor gray_in(1);

        bin_out(0)<= gray_in(3) xor gray_in(2) xor gray_in(1) xor gray_in(0);

    end process p1;
end behav;

```

Module No. M-ROU-06

```

library ieee;

use ieee.std_logic_1164.all;

```

```
use ieee.numeric_std.all;
```

```
entity fifo_controller is
```

```
    port (  
        reset, rdclk, wrclk, rreq, wreq: in std_logic ;  
        write_valid, read_valid: out std_logic;  
        wr_ptr, rd_ptr: out std_logic_vector (3 downto 0);  
        empty, full: out std_logic  
    );
```

```
end entity fifo_controller;
```

```
architecture behav of fifo_controller is
```

```
    component gray_counter is
```

```
        port  
        (  
            Clock, Reset, En: in std_logic;  
            count_out: out std_logic_vector(3 downto 0)  
        );
```

```
end component gray_counter;
```

```
for all: gray_counter use entity work.gray_counter(behav);
```

```
component gray_to_binary_convertor is
```

```
    Port ( gray_in : in STD_LOGIC_VECTOR (3 downto 0);  
          bin_out : out STD_LOGIC_VECTOR (3 downto 0)  
    );
```

```
end component gray_to_binary_convertor;
```

```
    for all: gray_to_binary_convertor use entity work.gray_to_binary_convertor(behav);
```

```
-- gray counters signals
```

```
signal read_counter, write_counter: std_logic_vector(3 downto 0);
```

```
-- binary counters signals
```

```
signal b_read_counter, b_write_counter: std_logic_vector(3 downto 0);
```

```
-- signals for write_valid and read_valid
```

```
signal read_signal, write_signal: std_logic;
```

```
    signal temp_empty, temp_full :std_logic;
```

```
begin
```

```

gray_read_counter: gray_counter port map (rdclk, reset, read_signal, read_counter);
gray_write_counter: gray_counter port map (wrclk, reset, write_signal, write_counter);

read_convertor: gray_to_binary_convertor port map (read_counter, b_read_counter);
write_convertor: gray_to_binary_convertor port map (write_counter, b_write_counter);

empty_full: process (rdclk, wrclk, reset, b_read_counter, b_write_counter) is
begin
if rdclk = '1' then
    if reset = '1' then
        temp_full <= '0';
        temp_empty <= '1';
    elsif b_write_counter = b_read_counter then
        temp_full <= '0';
        temp_empty <= '1';
    elsif unsigned(b_write_counter) + 1 = unsigned(b_read_counter) then
        temp_full <= '1';
        temp_empty <= '0';
    else
        temp_empty <= '0';
        temp_full <= '0';
    end if;
end if;
end process;

process (rdclk, rreq, temp_empty) is
begin
    if rdclk = '1' then
        if rreq = '1' and temp_empty = '0' then
            read_signal <= '1';
        else
            read_signal <= '0';
        end if;
    end if;
end process;

```

```

                end if;
            end if;
        end process;

        process (wrclk, wreq, temp_full) is
        begin
            if wrclk = '1' then
                if wreq = '1' and temp_full = '0' then
                    write_signal <= '1';
                else
                    write_signal <= '0';
                end if;
            end if;
        end process;

        read_valid <= read_signal;
        write_valid <= write_signal;
        empty <= temp_empty;
        full <= temp_full;
        wr_ptr <= b_write_counter;
        rd_ptr <= b_read_counter;
    end architecture behav;

```

Module No. M-ROU-07

```

library ieee;

use ieee.std_logic_1164.all;
use ieee.numeric_std.all;

entity fifo is
    port (
        reset, rdclk, wrclk, rreq, wreq: in std_logic ;
        data_in : in std_logic_vector(7 downto 0);

```

```

        data_out : out std_logic_vector(7 downto 0);
        empty, full: out std_logic
    );
end entity fifo ;

```

architecture behav of fifo is

component fifo_controller is

```

port (
    reset, rdclk, wrclk, rreq, wreq: in std_logic ;
    write_valid, read_valid: out std_logic;
    wr_ptr, rd_ptr: out std_logic_vector (3 downto 0);
    empty, full: out std_logic
);
end component fifo_controller ;

```

for all: fifo_controller use entity work.fifo_controller(behav);

component block_ram IS

```

PORT(
    d_in : IN std_logic_vector (7 downto 0);
    ADDRA,ADDRB :IN std_logic_vector (3 downto 0);
    WEA,REA,CLKA,CLKB :IN std_logic;
    d_out : OUT std_logic_vector (7 downto 0)
);

```

END component block_ram;

for all : block_ram use entity work.block_ram(behav);

signal write_valid, read_valid:std_logic;

signal wr_ptr, rd_ptr:std_logic_vector(3 downto 0);

begin

fc: fifo_controller port map (reset,rdclk, wrclk, rreq, wreq, write_valid, read_valid, wr_ptr, rd_ptr, empty, full);

rm: block_ram port map (data_in, wr_ptr, rd_ptr, write_valid, read_valid, wrclk, rdclk, data_out);

end architecture behav;

Module No. M-ROU-08

library ieee;

use ieee.std_logic_1164.ALL;

use ieee.numeric_std.ALL;

ENTITY round_robin IS

PORT (clock : IN std_logic;

din1,din2,din3,din4 : IN std_logic_vector (7 downto 0);

dout : OUT std_logic_vector (7 downto 0));

END;

ARCHITECTURE behave OF round_robin IS

TYPE state_type IS (d1,d2,d3,d4);

SIGNAL current_state: state_type := d1;

SIGNAL next_state: state_type;

BEGIN

clk:PROCESS (clock) IS

BEGIN

IF rising_edge(clock) THEN current_state <= next_state;

END IF;

END PROCESS clk;

ns: PROCESS (current_state, din1, din2, din3, din4) IS

BEGIN

CASE(current_state, din1, din2, din3, din4) IS

WHEN d1 =>

dout<=din1;

next_state <= d2;

WHEN d2 =>

dout<=din2;

next_state <= d3;

```

        WHEN d3 =>

            dout<=din3;

            next_state <= d4;

        WHEN d4 =>

            dout<=din4;

            next_state <= d1;

    END CASE;

END PROCESS ns;

END;
```

Module No. M-ROU-09

```

library ieee;

use ieee.std_logic_1164.all;

use ieee.std_logic_unsigned.all;

use ieee.numeric_std.all;

entity router is

    port(

        datai1, datai2, datai3, datai4: in std_logic_vector(7 downto 0);

        wr1, wr2, wr3, wr4: in std_logic;

        datao1, datao2, datao3, datao4: out std_logic_vector(7 downto 0);

        wrclk, rdclk: in std_logic;

        rst: in std_logic

    );

end entity router;
```

architecture behav of router is

```

    component reg IS

        port(Data_in : IN std_logic_vector (7 downto 0);

            Clock : IN std_logic;

            Data_out : OUT std_logic_vector (7 downto 0);

            Clock_En : IN std_logic;
```



```

        Reset : IN std_logic);

end component reg;

for all :reg use entity work.reg(behave);

component demux IS
PORT (
    Sel: IN std_logic_vector (1 downto 0);
    En : IN std_logic;
    d_in : IN std_logic_vector ( 7 downto 0);
    d_out1,d_out2,d_out3,d_out4 : OUT std_logic_vector (7 downto 0)
);

END component demux;

for all :demux use entity work.demux(behave);


component round_robin IS
PORT ( clock : IN std_logic;
din1,din2,din3,din4 : IN std_logic_vector (7 downto 0);
dout : OUT std_logic_vector (7 downto 0));

END component round_robin;

for all: round_robin use entity work.round_robin(behave);

component fifo is
    port (
        reset, rdclk, wrclk, rreq, wreq: in std_logic ;
        data_in : in std_logic_vector(7 downto 0);
        data_out : out std_logic_vector(7 downto 0);
        empty, full: out std_logic
    );
end component fifo;

    for all: fifo use entity work.fifo(behav);


type vector_array is array (0 to 3) of std_logic_vector(7 downto 0);
type vector_2d_array is array (0 to 3, 0 to 3) of std_logic_vector(7 downto 0);

```

```

type logic_2d_array is array (0 to 3, 0 to 3) of std_logic;

signal datai_arr, datao_arr, in_buff_out: vector_array;
signal demux_out, fifo_out: vector_2d_array;
signal wreq, empty, full: logic_2d_array;
    signal wr_arr: std_logic_vector(0 to 3);
begin

    datai_arr <= (datai1, datai2, datai3, datai4);
    wr_arr <= (wr1, wr2, wr3, wr4);

    g1: for i in 0 to 3 generate
        in_buf: reg port map (datai_arr(i), wrclk, in_buff_out(i), wr_arr(i), rst);
        demux_i: demux port map(in_buff_out(i)(1 downto 0), wr_arr(i), in_buff_out(i),
                                demux_out(i, 0), demux_out(i, 1), demux_out(i, 2),
demux_out(i, 3));
        scheduler: round_robin port map(rdclk, fifo_out(i,0), fifo_out(i, 1),
                                fifo_out(i, 2), fifo_out(i, 3), datao_arr(i));

    end generate g1;

    g2: for i in 0 to 3 generate
        g3: for j in 0 to 3 generate
            queue: fifo port map (rst, rdclk, wrclk, '1', wreq(j, i), demux_out(i, j),
                                fifo_out(j, i), empty(j, i), full(j, i));

        end generate g3;

    end generate g2;

    process(wrclk, rdclk, in_buff_out, datao_arr, wr_arr) is
    begin
        l1: for i in 0 to 3 loop
            l2: for j in 0 to 3 loop
                if (conv_integer(in_buff_out(j)(1 DOWNTO 0))) = i and wr_arr(j) = '1' THEN
                    wreq(i, j) <= '1';

```

```

                else
                    wreq(i, j) <= '0';
                end if;
            end loop l2;
        end loop l1;
    end process;

    datao1 <= datao_arr(0);
    datao2 <= datao_arr(1);
    datao3 <= datao_arr(2);
    datao4 <= datao_arr(3);

```

end architecture behav;

Module No. M-ROU-10

```

library ieee;

use ieee.std_logic_1164.ALL;

use ieee.numeric_std.ALL;

```

ENTITY testbench IS

END ENTITY;

ARCHITECTURE behave OF testbench IS

SIGNAL datai1,datai2,datai3,datai4,datao1,datao2,datao3,datao4 : std_logic_vector(7 DOWNT0 0);

SIGNAL wr1,wr2,wr3,wr4,wclock,rclock,rst : std_logic;

component Router is

```

    port(
        datai1, datai2, datai3, datai4: in std_logic_vector(7 downto 0);
        wr1, wr2, wr3, wr4: in std_logic;
        datao1, datao2, datao3, datao4: out std_logic_vector(7 downto 0);
        wrclk, rdclk: in std_logic;
        rst: in std_logic
    );

```

```

end component Router;

for dut: Router use entity work.Router(behav);

constant clock_period : time := 20 ns;

BEGIN

dut: Router port map( datai1, datai2, datai3, datai4,

                        wr1, wr2, wr3, wr4,

                        datao1, datao2, datao3, datao4,

                        wclock, rclock, rst);

wclk: PROCESS IS

BEGIN

    wclock <= '0';

    wait for clock_period / 2 ;

    wclock <= '1';

    wait for clock_period / 2 ;

END PROCESS wclk;


rclk: PROCESS IS

BEGIN

    rclock <= '0';

    wait for clock_period / 2 ;

    rclock <= '1';

    wait for clock_period / 2 ;

END PROCESS rclk;


p1: PROCESS IS

BEGIN

    rst <= '1';

    wait for clock_period;

    rst <= '0';

    wr1 <= '1';wr2 <= '1';wr3 <= '1';wr4 <= '1';

    datai1 <= "11001000";

    datai2 <= "10010001";

```

```

    datai3 <= "01010110";
    datai4 <= "10001011";
    wait for clock_period;
    datai1 <= "11011011";
    datai2 <= "10010000";
    datai3 <= "01110101";
    datai4 <= "10001110";
    wait for clock_period;
    datai1 <= "11011010";
    datai2 <= "10110011";
    datai3 <= "11110100";
    datai4 <= "00001001";
    wait for clock_period;
    datai1 <= "11001101";
    datai2 <= "11001010";
    datai3 <= "01010111";
    datai4 <= "10111100";

    wait;
END PROCESS p1;

assert_proc: PROCESS(datao1, datao2, datao3, datao4) IS
    BEGIN
        if datao1'event then
            assert datao1(1 downto 0) = "00" report "wrong output from port1 the address should be 00"
severity error;
        end if;
        if datao2'event then
            assert datao2(1 downto 0) = "01" report "wrong output from port2 the address should be 01"
severity error;
        end if;
        if datao3'event then
            assert datao3(1 downto 0) = "10" report "wrong output from port3 the address should be 10"
severity error;

```

```
        end if;

        if datao4'event then

            assert datao4(1 downto 0) = "11" report "wrong output from port4 the address should be 11"
severity error;

        end if;

    END PROCESS;


END ARCHITECTURE;
```

Appendix B


Module No. M-ROU-01 waveform




Module No. M-ROU-02 waveform

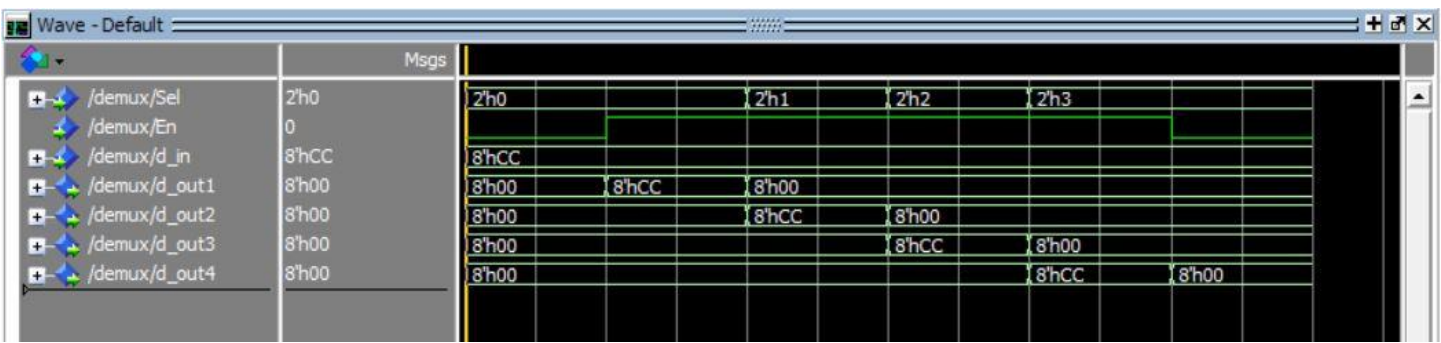


Module No. M-ROU-03 waveform

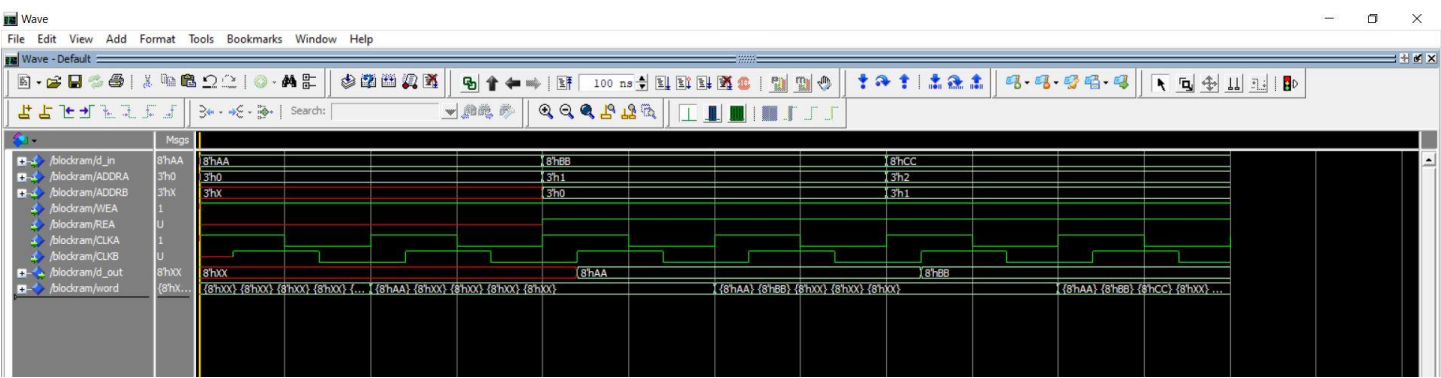


Module No. M-ROU-04 waveform

 

Module No. M-ROU-05 waveform

 


Module No. M-ROU-06 waveform

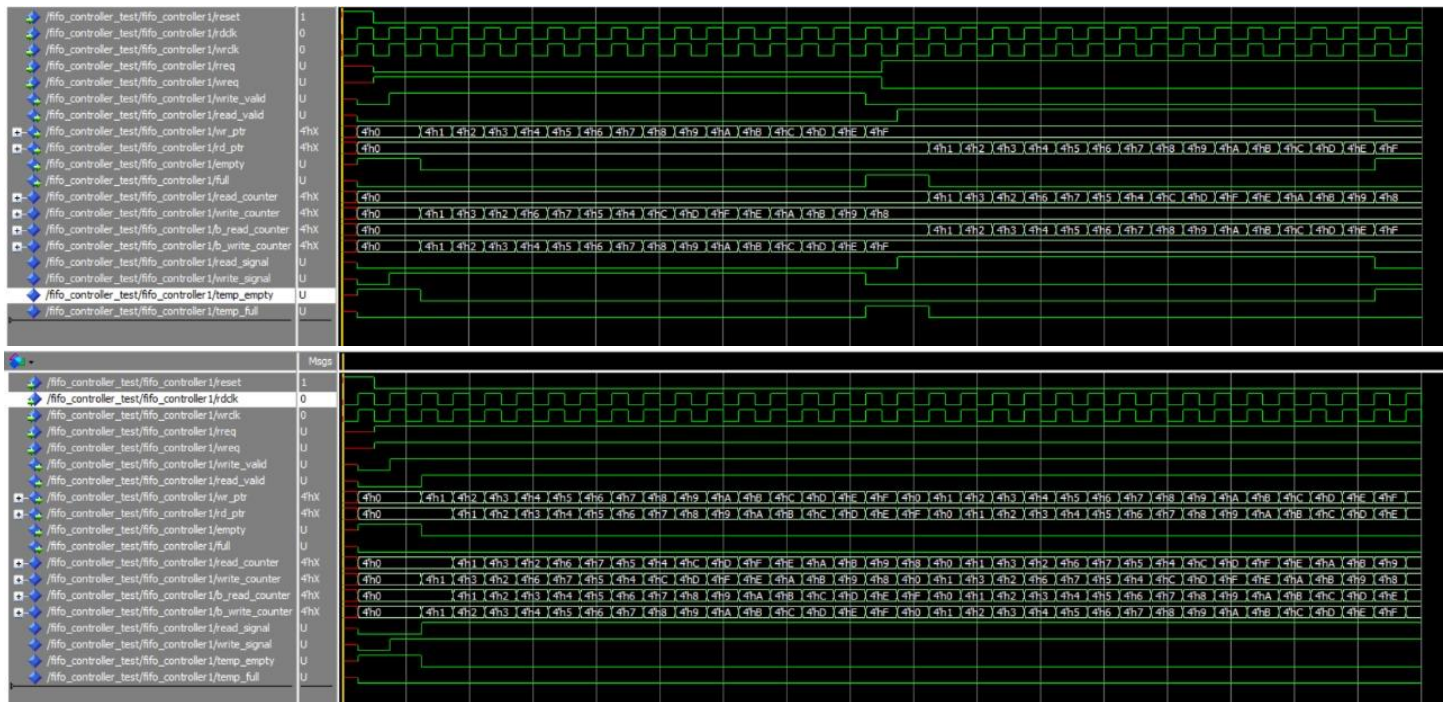


Module No. M-ROU-07 waveform



Module No. M-ROU-08 waveform

 

Module No. M-ROU-09 waveform

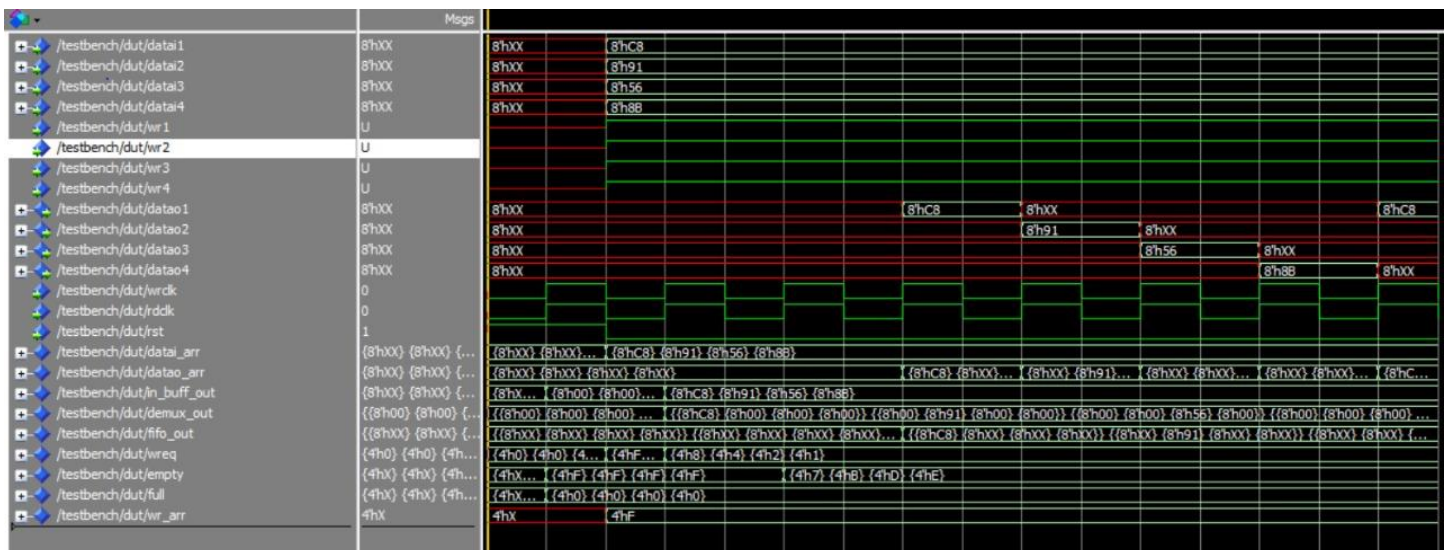

Module No. M-ROU-10 waveform

